

|                           |                          |
|---------------------------|--------------------------|
| Course Title:             | ELE302 Electric Networks |
| Course Number:            | ELE302                   |
| Semester/Year (e.g.F2016) | F2024                    |

|             |           |
|-------------|-----------|
| Instructor: | S. Jassar |
|-------------|-----------|

|                        |                   |
|------------------------|-------------------|
| Assignment/Lab Number: | 5                 |
| Assignment/Lab Title:  | Mutual Inductance |

|                  |              |
|------------------|--------------|
| Submission Date: |              |
| Due Date:        | NOV 22, 2024 |

| Student<br>LAST Name | Student<br>FIRST Name | Student<br>Number | Section | Signature*  |
|----------------------|-----------------------|-------------------|---------|-------------|
| Malik                | Hamza                 | 50112545          | 26      | Hamza Malik |
|                      |                       |                   |         |             |
|                      |                       |                   |         |             |

\*By signing above you attest that you have contributed to this written lab report and confirm that all work you have contributed to this lab report is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a "0" on the work, an "F" in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: <http://www.ryerson.ca/senate/current/pcl50.pdf>

# ELE 302

## Laboratory #5

### Mutual Inductance

## 1.0 INTRODUCTION:

When a time-varying current flows in a coil, it generates a time-varying magnetic flux in the space surrounding it. The time-varying magnetic flux induces a voltage in any conductor linked by this flux. Thus, if a second coil exists in a close physical proximity, an induced voltage will be generated across its terminals; its value is related to the time-varying current in the first coil by a parameter known as mutual inductance. Although the coils are physically separate, their interaction is due to the magnetic coupling that exists between them. The practical application of magnetic-coupling is important, especially in electrical power systems and communication systems.

## 2.0 OBJECTIVES:

- To determine the dot-convention of a given magnetically-coupled set.
- To measure the resistive and inductive parameters of the set.
- To verify the measured-value of the mutual inductance of the set by using an alternative method: measurement of mutual inductance as a function of self-inductance.
- To examine the concept of impedance reflection between magnetically-coupled networks.

## 3.0 REQUIRED LAB EQUIPMENT & PARTS:

- Function Generator (FG) and Oscilloscope.
- ELE202 Lab Kit and ELE302 Lab Kit: various components, breadboard, wires and jumpers.
- Magnetically-Coupled Coils (from your TA).

## 4.0 PRE-LAB ASSIGNMENT (3 marks with 1.5 marks for each step):

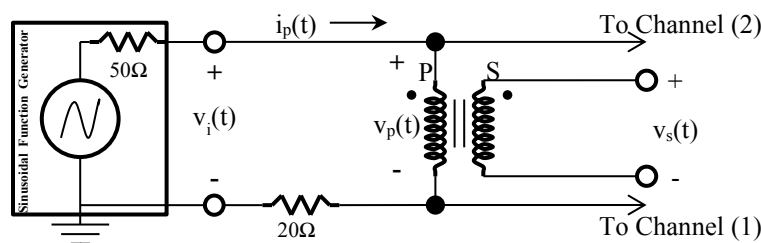




Figure 1.0: Measuring Parameters of Magnetically-Coupled Coils

- (a) Step 1: The circuit shown in **Figure 1.0** consists of magnetically-coupled coils, where the primary coil is connected in series with a sinusoidal source and a current-sampling  $20\Omega$ -resistor, while the secondary coil is open-circuit; i.e., has no load (NL).

The primary coil has self-inductance  $L_p$  and inherent resistance  $R_p$ , and the secondary coil has self-inductance  $L_s$  and inherent resistance  $R_s$ ; the mutual inductance between the two coils is  $M$ .

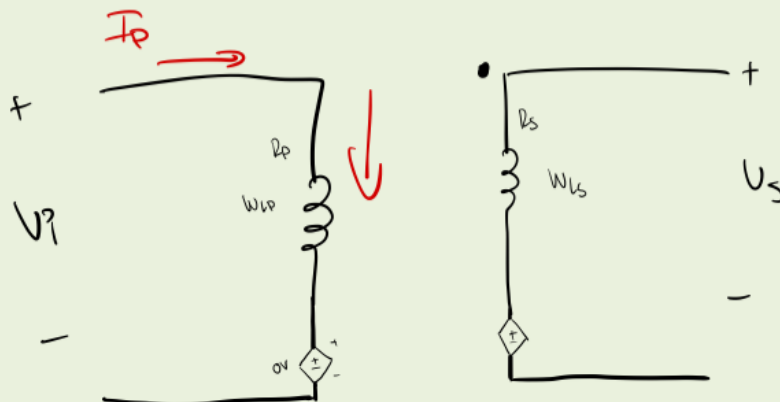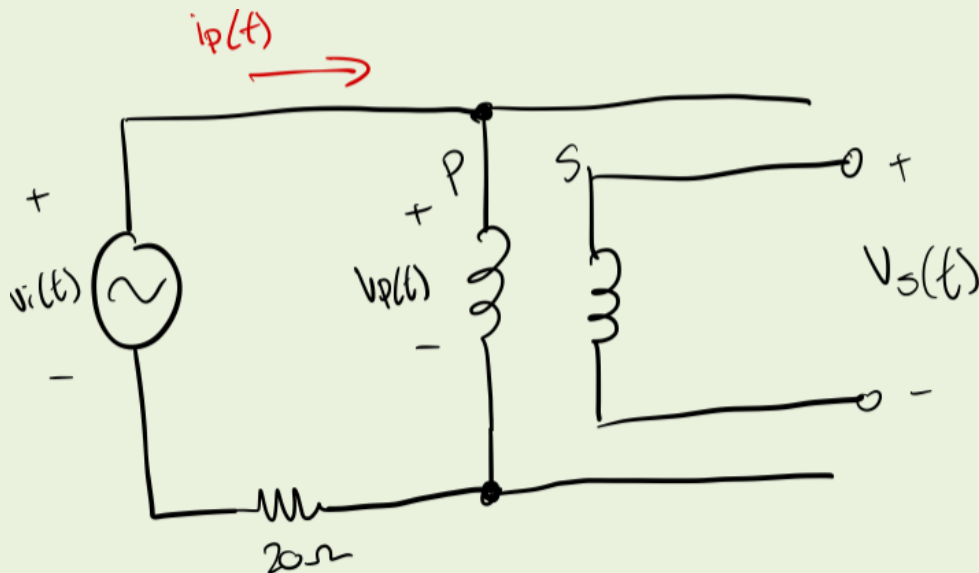- i) Determine the expressions for  $V_i$  and  $V_s$  in terms of  $I_p$  and the coils parameters, where  $V_i$ ,  $V_s$  and  $I_p$  are the phasors for  $v_i(t)$ ,  $v_s(t)$  and  $i_p(t)$ , respectively.

Pre-Lab workspace (show your analysis here)



$$-V_i + j\omega L_p I_p + R_p I_p = 0$$

$$V_i = (j\omega L_p + R_p) I_p$$

$$V_s = j\omega M I_p$$


$$V_p = j\omega L_p I_p$$

$$-V_s + j\omega M I_p = 0$$

The  $I_p$  current flows on primary side. The dot represents the secondary side

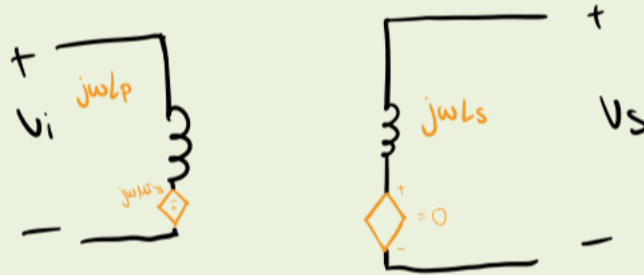- ii) Suppose that the primary and secondary coils are interchanged; i.e., the primary terminals are now open circuited, and the current flow through  $L_s$  is  $i_s(t)$ . Find the expressions for  $V_i$  and  $V_p$  in terms of  $I_s$  and the coils parameters, where  $V_i$ ,  $V_s$  and  $I_s$  are the phasors for  $v_i(t)$ ,  $v_s(t)$  and  $i_s(t)$ , respectively.

Pre-Lab workspace (show your analysis here)



$$V_p = 0$$

$$-V_i - j\omega M I_s = 0$$

$$V_i = -j\omega M I_s$$

$$j\omega L_s I_s + V_s + R_s I_s = 0$$

$$V_s = -I_s (j\omega L_s + R_s)$$


When current is opposite:

$$-V_i + j\omega M I_s = 0$$

$$V_p = j\omega M I_s$$

$$-V_s + (j\omega L_s + R_s) I_s = 0$$

$$V_s = (j\omega L_s + R_s) I_s$$

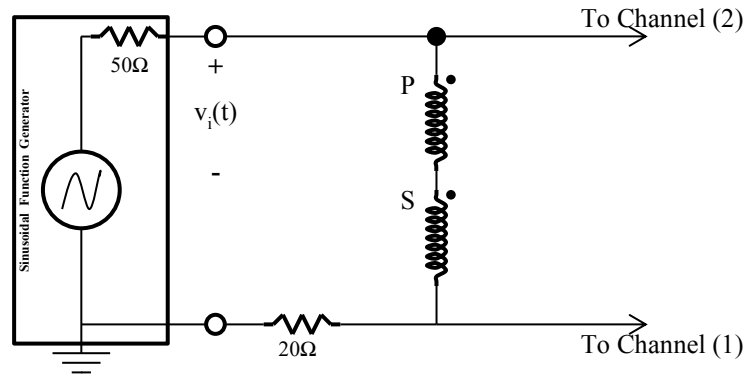

**Figure 2.0:** Measuring Mutual Inductance as Self-Inductance

- (b) Step 2: The primary and secondary coils shown in **Figure 2.0** are connected in series-aiding with the current  $i(t)$  entering each of the coils from its dotted terminal. Let the total inductance of this arrangement be  $L_A$ . Upon interchanging the secondary terminals connections, however, total inductance of the series-opposing arrangement becomes  $L_B$ .

Show that the mutual inductance  $M$  is:

$$M = \frac{L_A - L_B}{4}$$

*Pre-Lab workspace (show your analysis here)*

$$-v_i(t) + v_i(t) + L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + M \frac{di}{dt} + M \frac{di}{dt} = 0$$

$$(L_1 + L_2 + 2M) \frac{di}{dt} = v_i(t) - v_i(t)$$

$$(L_1 + L_2 + 2M) = \frac{v_i(t)}{\frac{di}{dt}} - \frac{v_i(t)}{\frac{di}{dt}}$$

$$L_1 + L_2 + 2M = L_A - \frac{v_i(t)}{\frac{di}{dt}}$$

$$(L_1 + L_2 - 2M) \frac{di}{dt} = v_i(t) - v_i(t)$$

$$(L_1 + L_2 - 2M) = L_B - \frac{v_i(t)}{\frac{di}{dt}}$$

$$L_A - L_B = 4M$$

$$M = \frac{L_A - L_B}{4}$$