

Course Title:	ELE302 Electric Networks
Course Number:	ELE302
Semester/Year (e.g.F2016)	F2024





Instructor:	S. Jassar
-------------	-----------

Assignment/Lab Number:	3
Assignment/Lab Title:	Frequency Response and Bode Plots Postlab

Submission Date:	
Due Date:	

Student LAST Name	Student FIRST Name	Student Number	Section	Signature*
Malik	Hamza	501112545	26	Hamza Malik

\*By signing above you attest that you have contributed to this written lab report and confirm that all work you have contributed to this lab report is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a "0" on the work, an "F" in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: <http://www.ryerson.ca/senate/current/pol60.pdf>

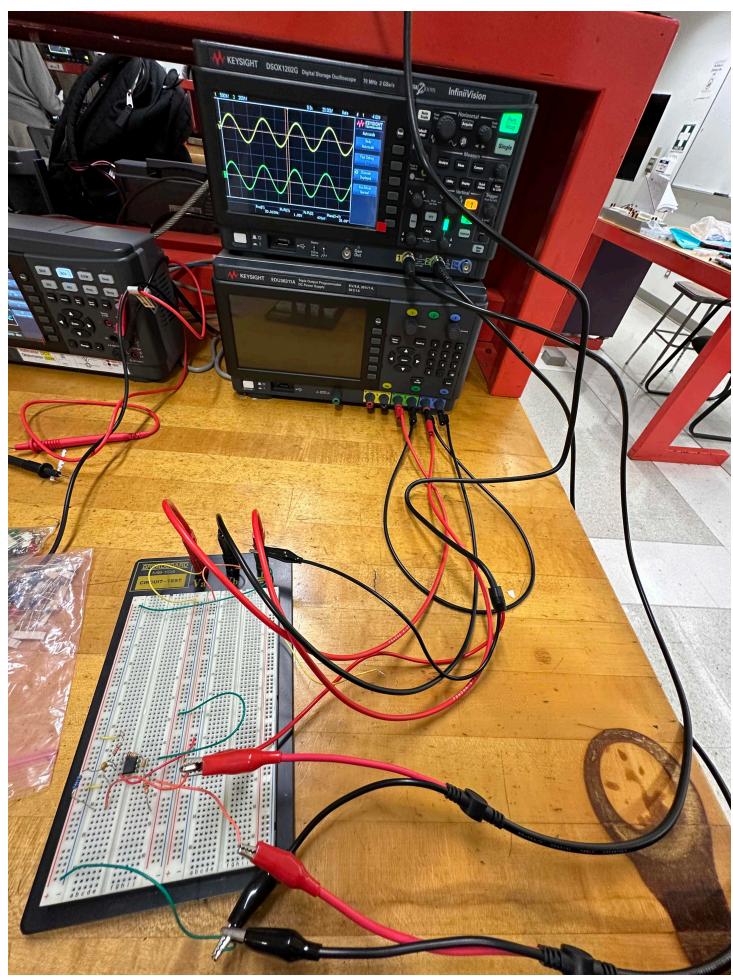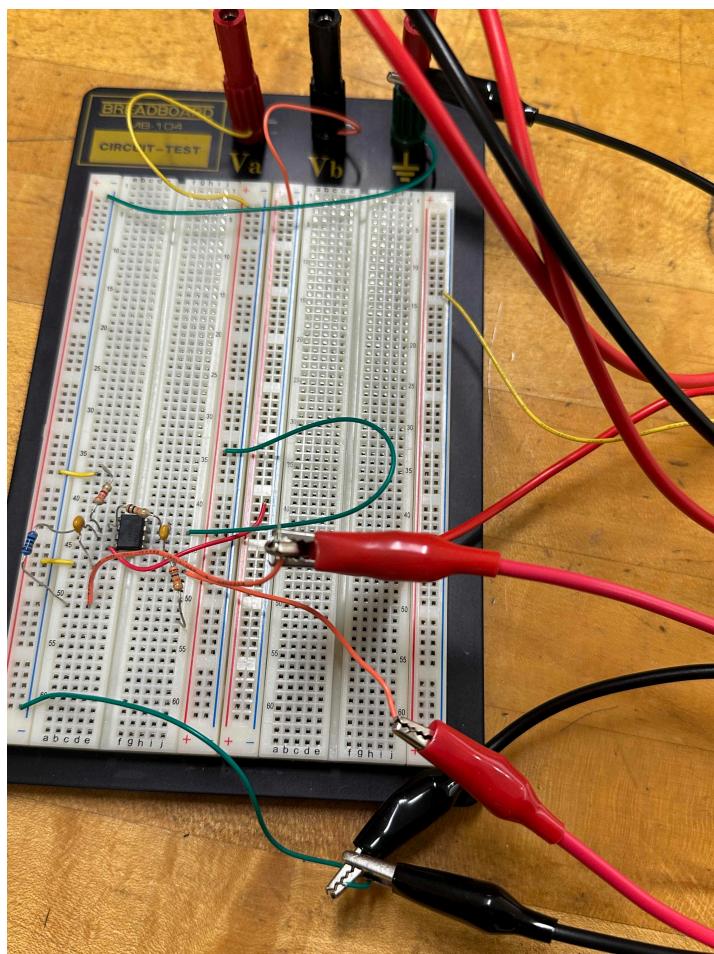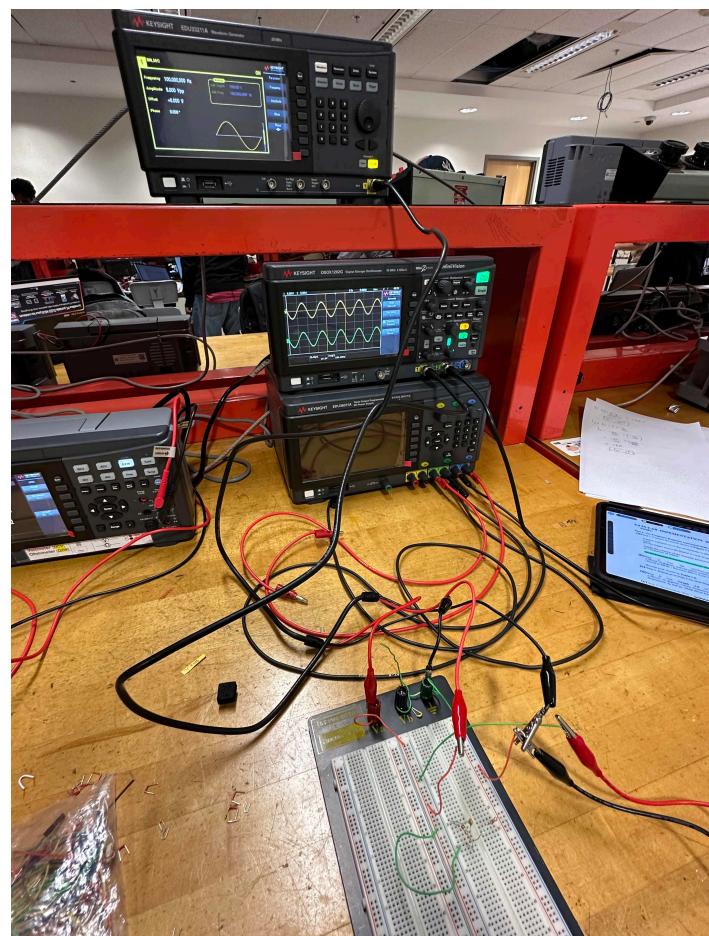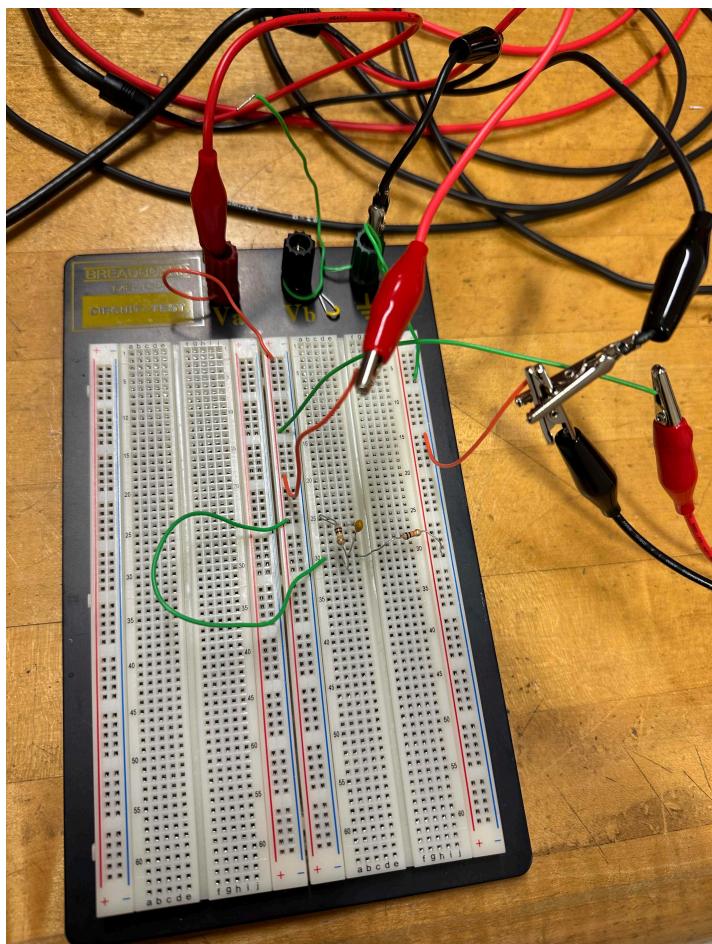

## 5.0 IN-LAB IMPLEMENTATION & MEASUREMENTS (5 marks in total):

**Part I: The Frequency Response Associated With [One Pole-One Zero] Transfer Function**

- (a) Step 1: Connect the circuit shown in **Figure 1.0**.

Connect Channel (1) of the oscilloscope to display  $v_i(t)$  and Channel (2) of the oscilloscope to display  $v_o(t)$ .

Set the trigger source → Channel (1) and Acquire Mode → Averaging.

Adjust the controls of the function generator to provide a **sinusoidal** input voltage  $v_i(t)$  of **5V (peak)** at a frequency of **100Hz**.

**On the Function Generator: Waveform: Sine wave, Amplitude: 5 VPP, Frequency: 100 Hz**

- (b) Step 2: Use the oscilloscope displays to measure the phase angle  $\angle H(\omega)^o$  in degrees, and use either oscilloscope or DMM to measure  $V_i$  and  $V_o$ . Evaluate the magnitude  $|H(\omega)|$  in dB as:  $|H(\omega)|(\text{in dB}) = [V_o(\text{in dB}) - V_i(\text{in dB})]$ .

Record your results in **Table 1.0**.


- (c) Step 3: Repeat as in Step 2 for each frequency setting in **Table 1.0**.

- (d) Step 4: Use **Graph 3.0** to plot the magnitude  $|H(\omega)|$  in dB and phase  $\angle H(\omega)^o$  in degrees versus frequency in Hz. Use your plot to determine the locations of the corner frequencies:  $f_Z$  and  $f_P$ . Mark these frequencies on **Graph 3.0**.

- (e) Step 5: Demonstrate Step 1 to Step 4 to your TA. (1 mark)

**Table 1.0 (0.5 marks)**

Frequency (Hz)	$ V_o  (\text{dB})$	$ V_i  (\text{dB})$	$ H(\omega)  (\text{dB})$	$\angle H(\omega) (\text{degrees})$
20	-7.57	13.17	-20.76	28.7
50	-6.76	13.17	-19.93	30.5
100	-4.87	13.17	-18.04	33.4
200	-1.086	13.17	-14.256	47.6
500	5.277	13.17	-7.893	58.9
1K	9.355	13.13	-3.775	52.4
2K	11.737	13.12	-1.38	40.6
10K	13.0	13.12	-0.119	9.21
20K	13.065	13.12	-0.0549	6.43
50K	13.08	13.12	-0.0399	3.21
100K	13.127	13.12	-0.007	0.51

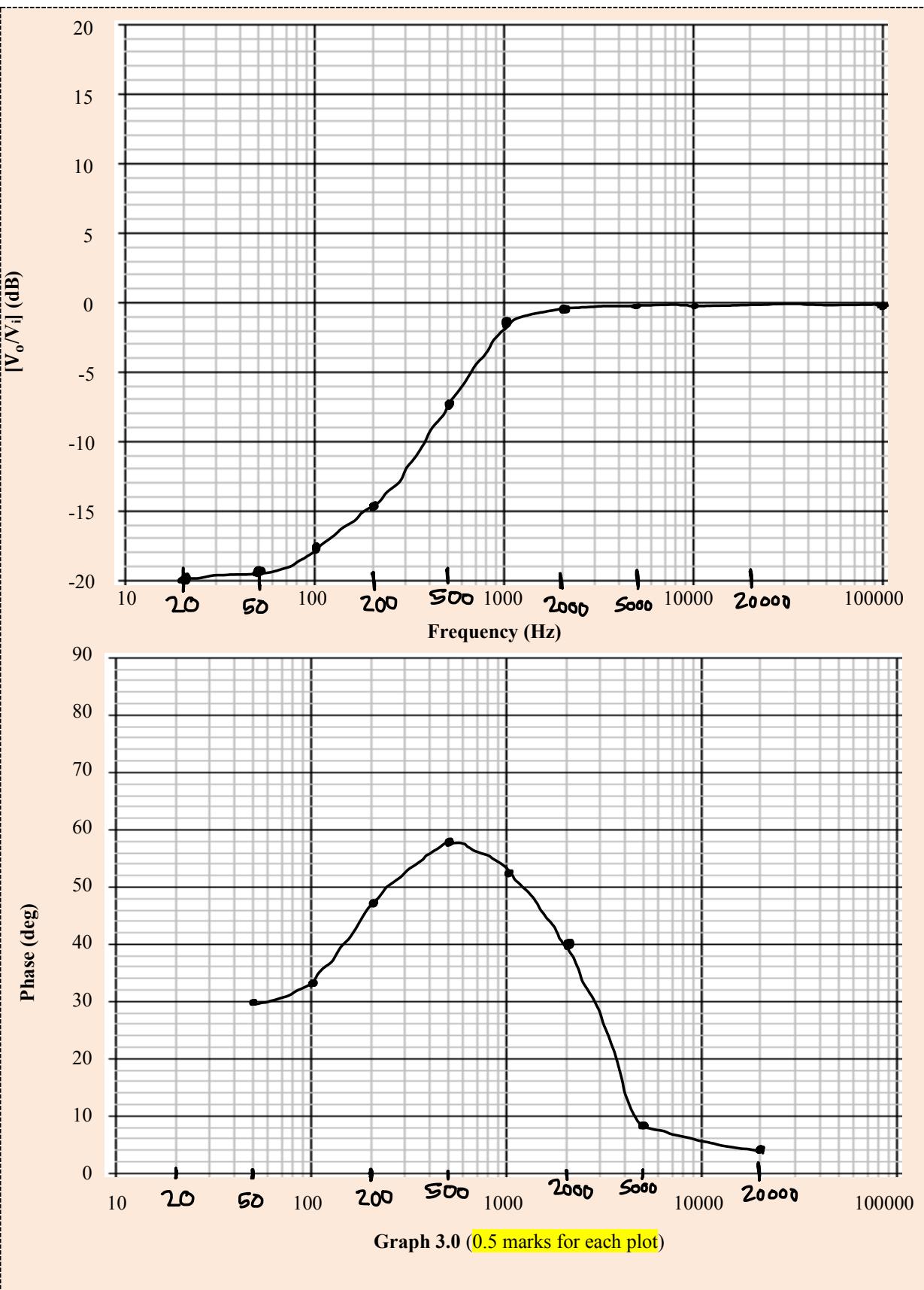

## Part II: The Frequency Response Associated with [Two Poles-One Zero] Transfer Function


- (f) Step 6: Connect the circuit shown in **Figure 2.0**. Connect Channel (1) of the oscilloscope to display  $v_i(t)$  and Channel (2) of the oscilloscope to display  $v_o(t)$ ; set the trigger source → Channel (1). Adjust the controls of the function generator to provide a **sinusoidal** input voltage  $v_i(t)$  of **0.5V (peak)** at a frequency of 100Hz.

On the Function Generator: Waveform: Sine wave, Amplitude: 0.5 VPP, Frequency: 100 Hz


- (g) Step 7: Repeat the measurements as in Step 2 and Step 3, and record your results in **Table 2.0**.
- (h) Step 8: Use **Graph 4.0** to plot the magnitude  $|H(\omega)|$  in dB and phase  $\angle H(\omega)$  in degrees versus frequency in Hz. Use your plots to determine the locations of the corner frequencies:  $f_{P1}$  and  $f_{P2}$ . Mark these frequencies on **Graph 4.0**.
- (i) Step 9: Demonstrate Step 6 to Step 8 to your TA. (1 mark)

**Table 2.0 (0.5 marks)**

Frequency (Hz)	$ V_o $ (dB)	$ V_i $ (dB)	$ H(\omega) $ (dB)	$\angle H(\omega)$ (degrees)
20	-29.742	-6.8	-31.542	87.5°
50	-16.565	-6.8	-23.365	85.64°
100	-10.665	-6.8	-17.465	77.65°
200	-5.023	-6.8	-11.823	69.39°
500	1.072	-6.8	-5.728	4.46°
1K	3.571	-6.8	-3.289	19.65°
2K	4.247	-6.8	-2.553	-2.25°
10K	-6.576	-6.8	-7.376	-59.04°
20K	-5.56	-6.8	-12.36	-79°
50K	-13.485	-6.8	-20.285	-97.24°
100K	-10.61	-6.8	-17.41	-96.22

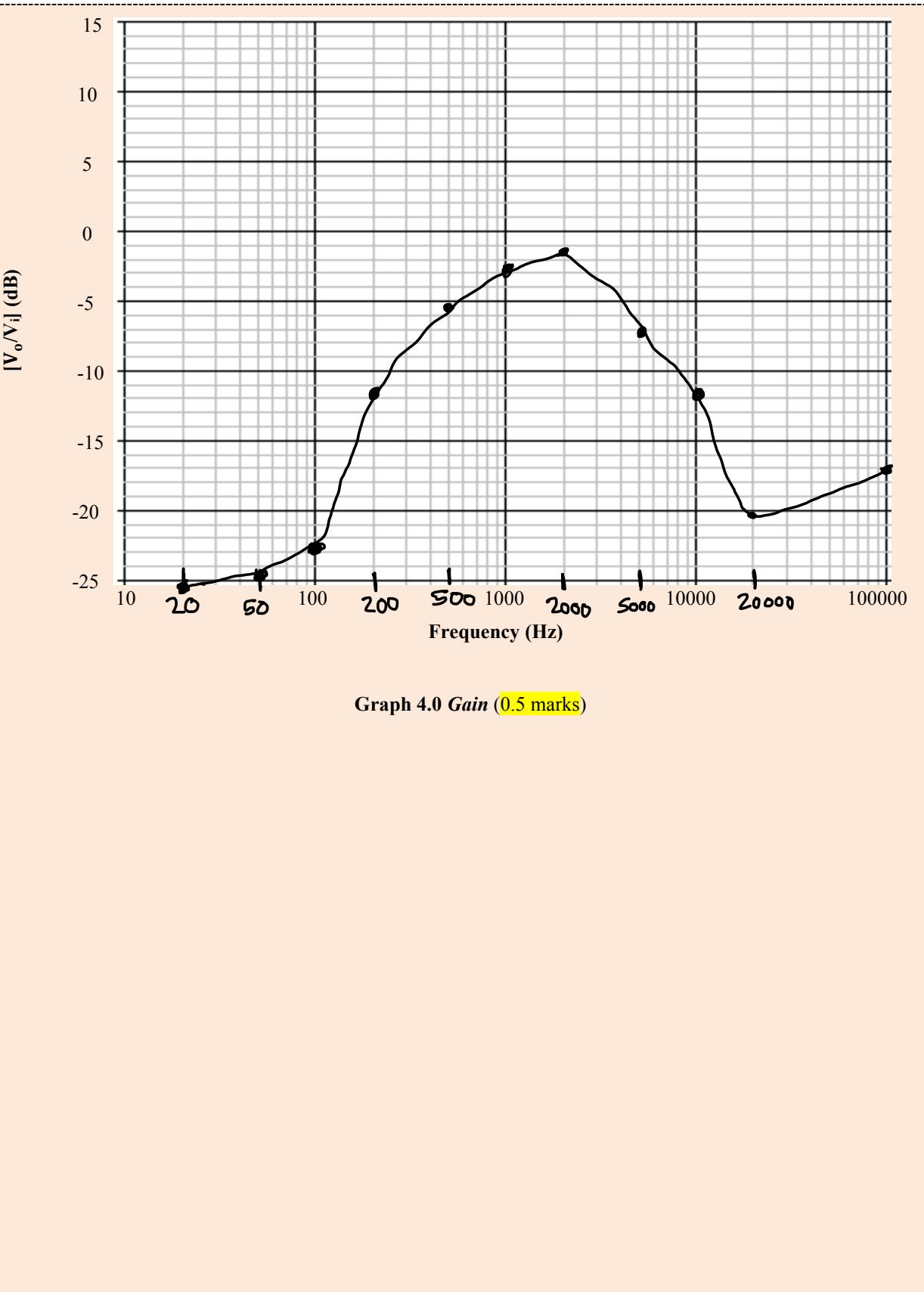

Graph 4.0 Gain (0.5 marks)

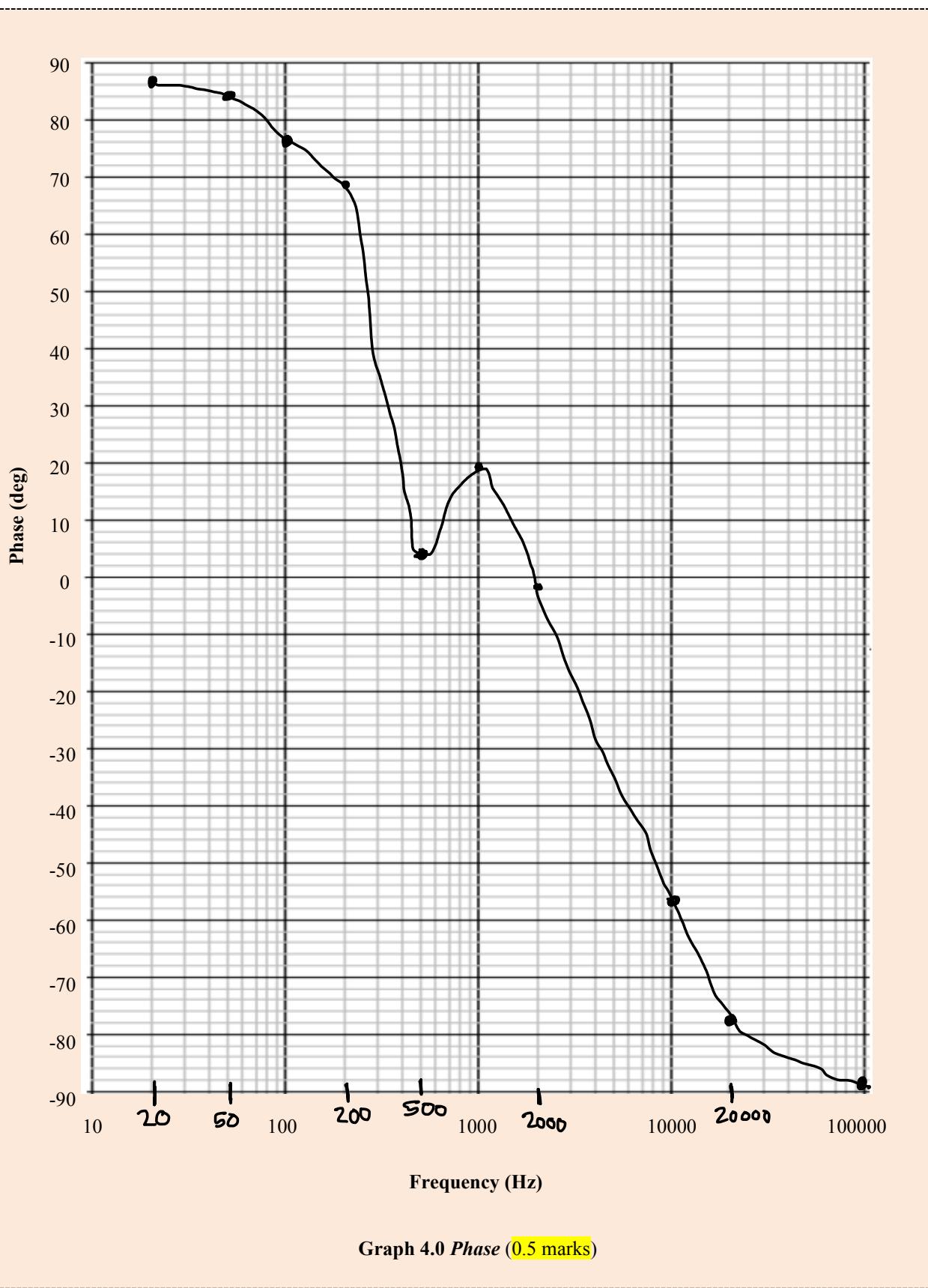

## 6.0 POST-LAB QUESTIONS (2 marks in total, 2/3 marks for each question):

- (1) By considering all the asymptotic & measured plots, answer the following:
- At which frequencies does the asymptotic plot yield the maximum error? What would you do to minimize this error?
  - At what frequency range does the error become negligible?

a) The frequency with max error is 500Hz. As the numbers are increasing it goes from steady increase and jumps here. For instance, at 200Hz it was -6.44 then at 500Hz it became -0.213Hz. I would add a few extra points in between to keep a steady increase.

b) The error becomes negligible after 1K to look. This is where it becomes steady increase

(2) What is the maximum rate of attenuation of  $|H(\omega)|$  in dB/decade for your plots on in **Graph 3.0?**

$$m = \frac{y_2 - y_1}{x_2 - x_1}$$

$m$  = slope of  
line

$$m = \frac{28 - 9}{\log_{10} 100 - \log_{10} 20}$$
$$= 34.2$$

$\therefore$  The max rate of attenuation  
will be 34.2

- (3) By considering your plots on **Graph 4.0**, answer the following:
- What is the maximum rate of attenuation of  $|H(\omega)|$  in dB/decade?
  - Suppose that the  $2.7\text{k}\Omega$  resistor and the  $0.01\mu\text{F}$  capacitor at the input part of the circuit in **Figure 2.0** were interchanged, what effect would this have on the frequency-response characteristics?

$$\begin{aligned} a) m &= \frac{y_2 - y_1}{x_2 - x_1} \\ &= \frac{77.4 - 87.4}{\log_{100} - \log_{20}} \\ &= -14.3 \end{aligned}$$

$\therefore$  The max rate  
of attenuation  
of graph  
4.0 will  
be  $-14.3$

b) If the capacitor and resistor  
were switched this will result  
into an extra zero in  
the transfer function  
This is due to the fact  
that the capacitor is now  
directly connected to the  
input voltage.